

## Part 1: Diff. Eq & Matrix Formulation

```
%{
N1:    i1 + i2 = 0
        i1 + [(V1-V2)/R1 + C(d(V1-V2)/dt)] = 0
        V1 = Vin (1)
N2:    i2 + i3 + i4 = 0
        [(Vin-V2)/R1 + C(d(Vin-V2)/dt)] + V2/R2 + iL (2)
N3:    iL + i3 = 0
        iL + V3/R3 = 0 (3)
N4:    alpha*i3 + i4 = 0
        alpha*i3 + (V4-V5)/R4 = 0 (4)
        V4 = alpha*i3 (5)
N5:    i4 + i0 = 0
        (V5-V4)/R4 + V0/R0 = 0 (6)

N1:
        i1 + [(V1-V2)G1 + (V1-V2)sC] = 0 (1)
        V1 = Vin (2)
N2:
        [(V2-V1)G1 + (V2-V1)sC] + V2G2 + (V2-V3)sL (3)
N3:
        (V3-V2)sL + V3G3 = 0 (4)
N4:
        alpha*i3 + (V4-V5)G4 = 0 (5)
        V4 = alpha*i3 (6)
N5:
        (V5-V4)G4 + V0G0 = 0 (7)
Where s = jw
V1,      V2, iL,      V3,      V4,      Vo  <-- V matrix
G:
        1,      0,  0,      0,      0,      0
    -G1, G1+G2,  0,      0,      0,      0
        0,      1,  0,     -1,      0,      0
        0,      0, -1,      G3,      0,      0
        0,      0,  0,  -a*G3,      1,      0
        0,      0,  0,      0,     -G4, G4+G0

C:
        0,      0,  0,  0,      0,  0,
    -C,      C,  0,  0,      0,  0,
        0,      0,  L,  0,      0,  0,
        0,      0,  0,  0,      0,  0,
        0,      0,  0,  0,      0,  0,
        0,      0,  0,  0,      0,  0,

%}

clear all
close all
clc
```

---

```

G = zeros(6, 6);

%Conductances(1/R):
G1 = 1;
G2 = 0.5;
G3 = 0.1;
G4 = 10;
G0 = 0.001;

%Additional Parameters:
alpha = 100;
Cval = 0.25;
L = 0.2;
vin = zeros(1, 20);
vo = zeros(1, 20);
v3 = zeros(1, 20);

G(1, 1) = 1; % 1
G(2, 1) = -G1; G(2, 2) = G1 + G2; % 2
G(3, 2) = -1; G(3, 4) = 1; % iL
G(4, 3) = -1; G(4, 4) = G3; % 3
G(5, 5) = 1; G(5, 4) = -alpha*G3; % 4
G(6, 6) = G4 + G0; G(6, 5) = -G4; % 5

C = zeros(6);

C(2, 1) = -Cval; C(2, 2) = Cval;
C(3, 3) = L;

```

The C and G matrices were set as follows:

C  
G

C =

0	0	0	0	0	0
-0.2500	0.2500	0	0	0	0
0	0	0.2000	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0

G =

1.0000	0	0	0	0	0
-1.0000	1.5000	0	0	0	0
0	-1.0000	0	1.0000	0	0
0	0	-1.0000	0.1000	0	0
0	0	0	-10.0000	1.0000	0
0	0	0	0	-10.0000	10.0010

---

The input was swept as a DC input from -10V to 10V. Both the output voltage and the voltage, V3, were plotted over this DC sweep.

```
F = zeros(1, 6);
v = -10;



for i = 1:21
    vin(i) = v;
    F(1) = vin(i);

    Vm = G\F';

    vo(i) = Vm(6);
    v3(i) = Vm(4);
    v = v + 1;
end

figure(1)
plot(vin, vo);
title('VO for DC Sweep (Vin): -10 V to 10 V');
xlabel('Vin (V)');
ylabel('Vo (V)')

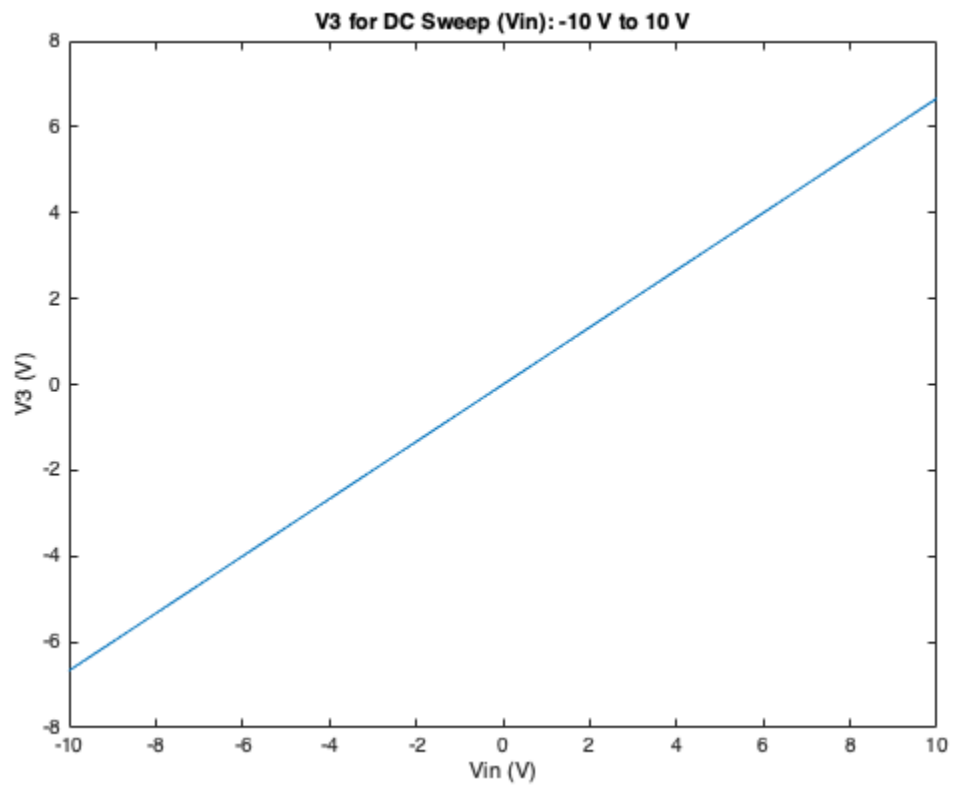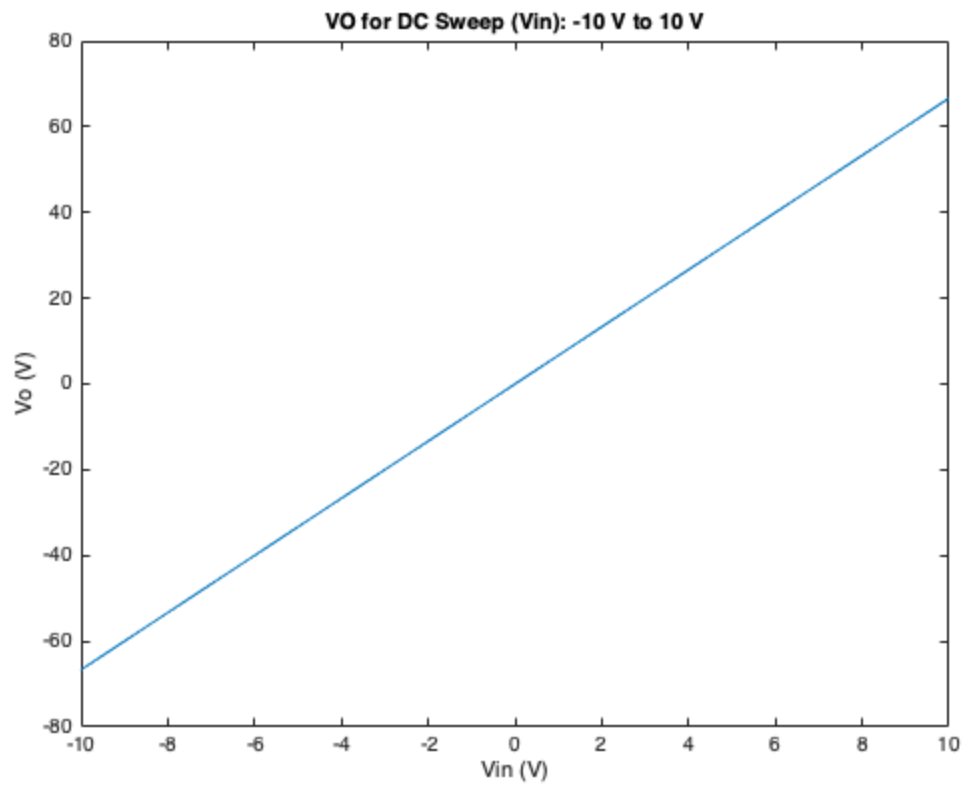figure(2)
plot(vin, v3);
title('V3 for DC Sweep (Vin): -10 V to 10 V');
xlabel('Vin (V)');
ylabel('V3 (V)')
```



---



Next,  $V_o$  was analyzed for an AC case. Therefore, the output was plotted against the angular frequency, and the dB gain was plotted.

```
F(1) = 1;
vo2 = zeros(1, 1000);
freq = linspace(0, 1000, 1000); % note: in radians
Av = zeros(1, 1000);
Avlog = zeros(1, 1000);

for i = 1:1000
    Vm2 = (G+1i*freq(i)*C)\F';
    vo2(i) = Vm2(6);
    Av(i) = vo2(i)/F(1);
    Avlog(i) = 20*log10(Av(i));
end
figure(3)
plot(freq, Av)
title('Vo(w) (part C)')
xlabel('w (rad)')
ylabel('Av (V/V)')

figure(4)
semilogx(freq, Avlog)
xlim([0 1000])
title('Vo(w) dB (part C)')
xlabel('w (rad)')
ylabel('Av (dB)')
```

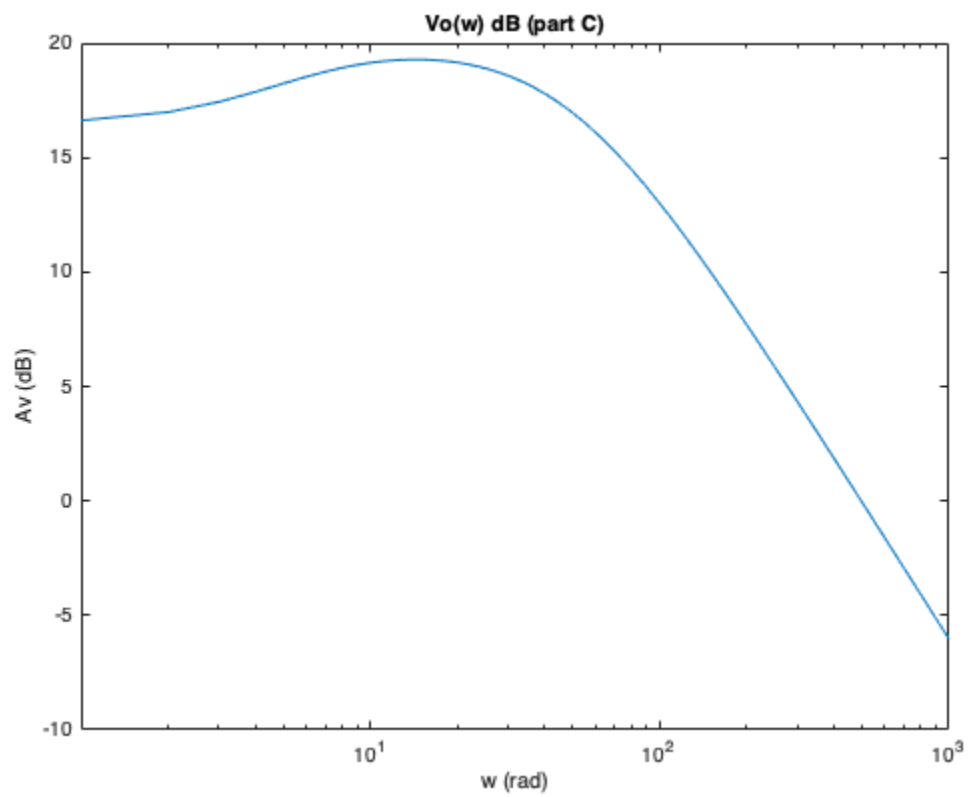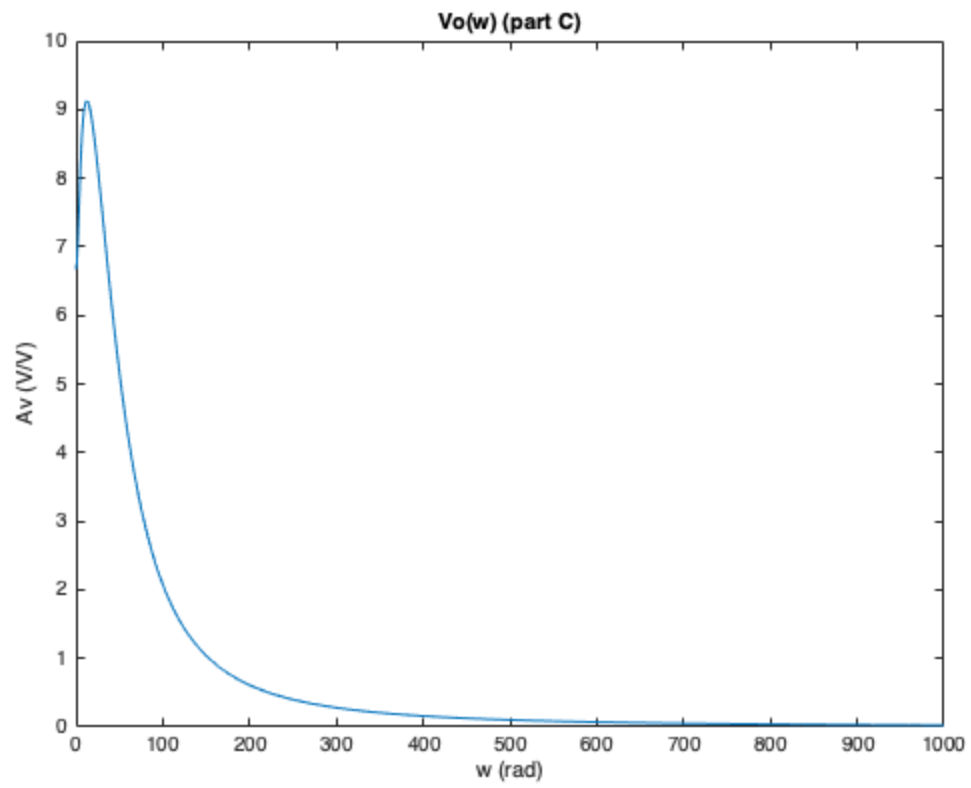*Warning: Imaginary parts of complex X and/or Y arguments ignored*  
*Warning: Imaginary parts of complex X and/or Y arguments ignored*



---

The AC case was plotted again where the gain was plotted as function of random perturbations on C using a normal distribution with std = .05 at  $w = \pi$ . A histogram was made to demonstrate the changes in the gain.

```
w = pi;
Av2 = zeros(15, 1);
Cper = zeros(15, 1);
vo3 = zeros(1, 15);



for i = 1:1000
    C(2, 1) = normrnd(-Cval, 0.05);
    C(2, 2) = normrnd(Cval, 0.05);
    C(3, 3) = normrnd(L, 0.05);
    Vm3 = (G+1i*w*C)\F';
    vo3(i) = Vm3(6);
    Av2(i) = vo3(i)/F(1);
end

figure(5)
hist(real(Av2), 25)
title('Gain Distribution for Normal Perturbations in C matrix')
xlabel('Gain at w = pi')
```



Assignment4Transient  
Assignment4Noiseandnon



$C =$



0	0	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0.2000	0	0	0	0
0	0	0	0.0000	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

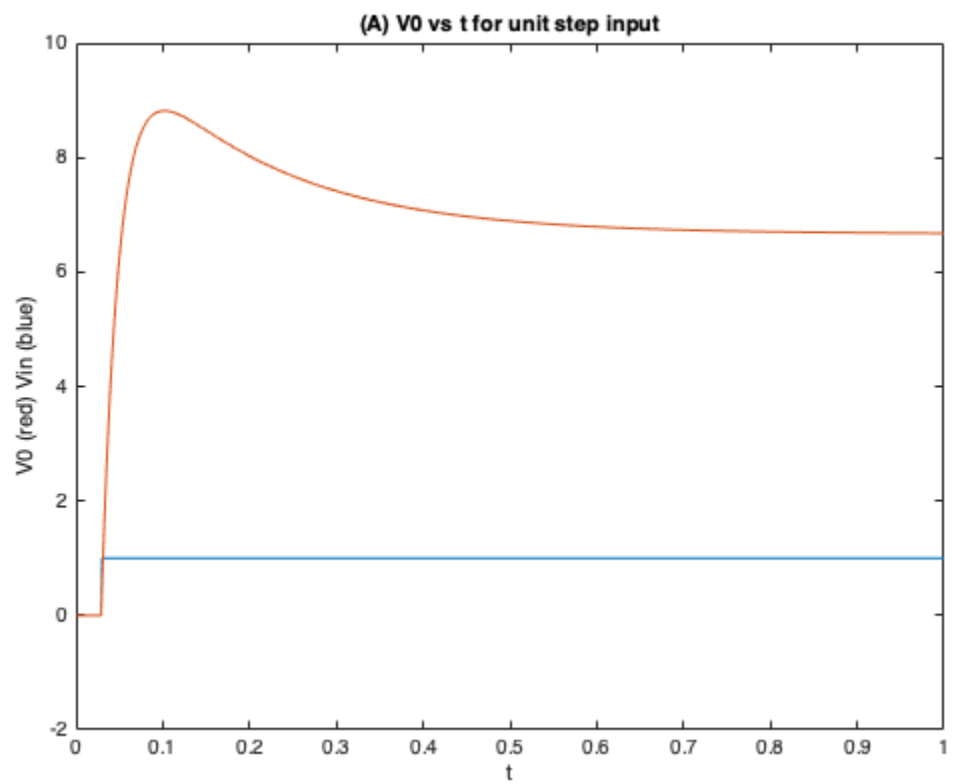
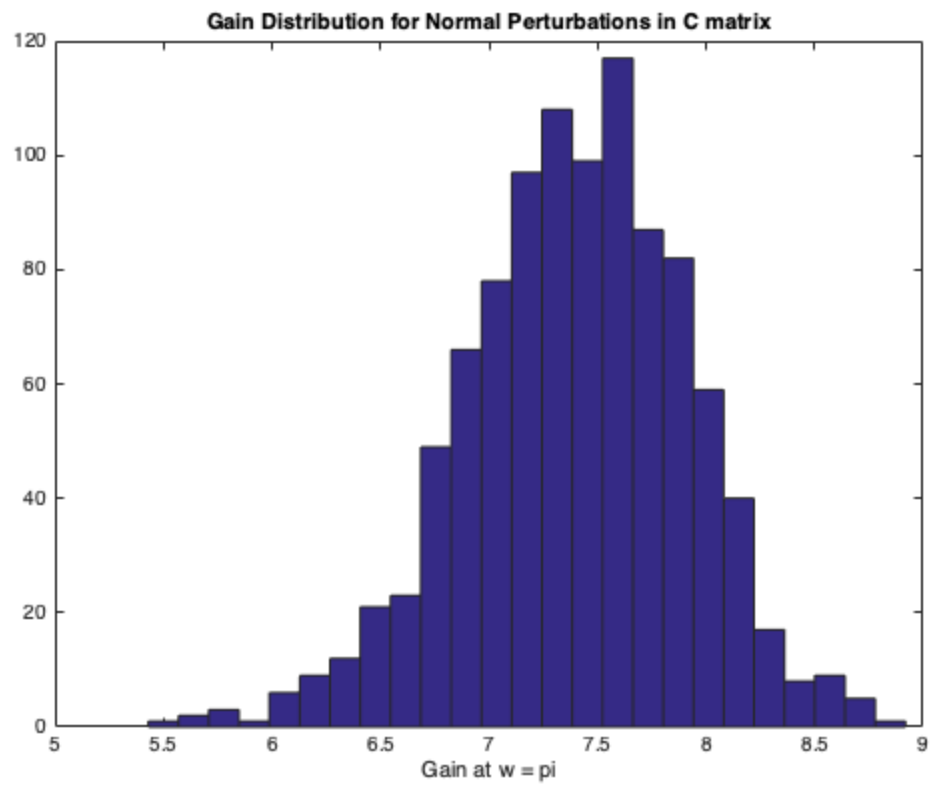





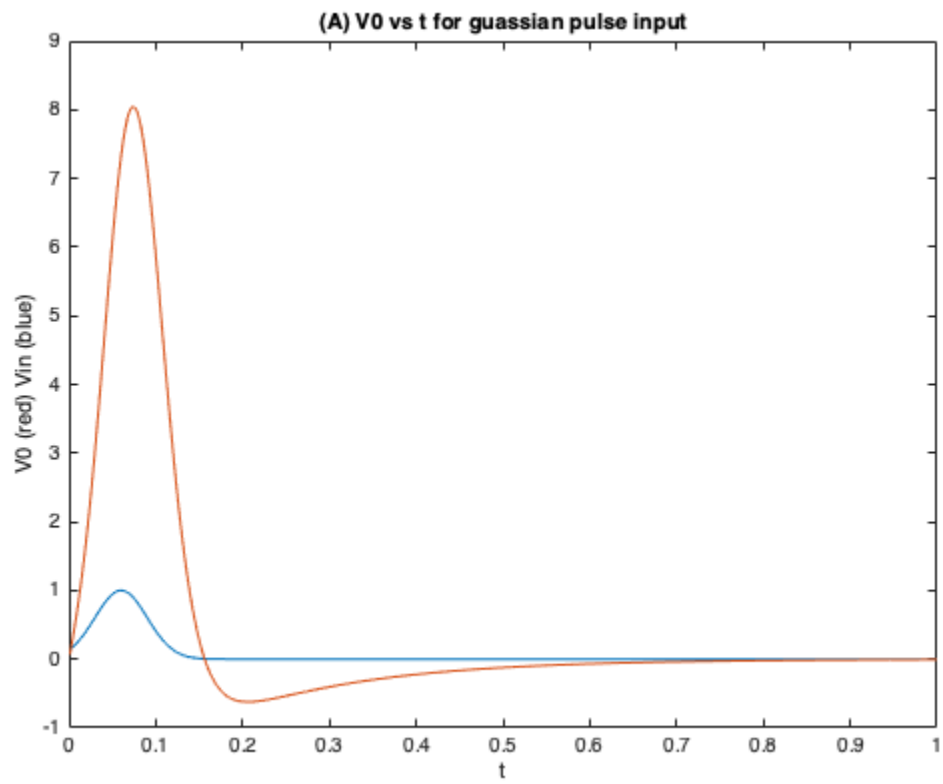
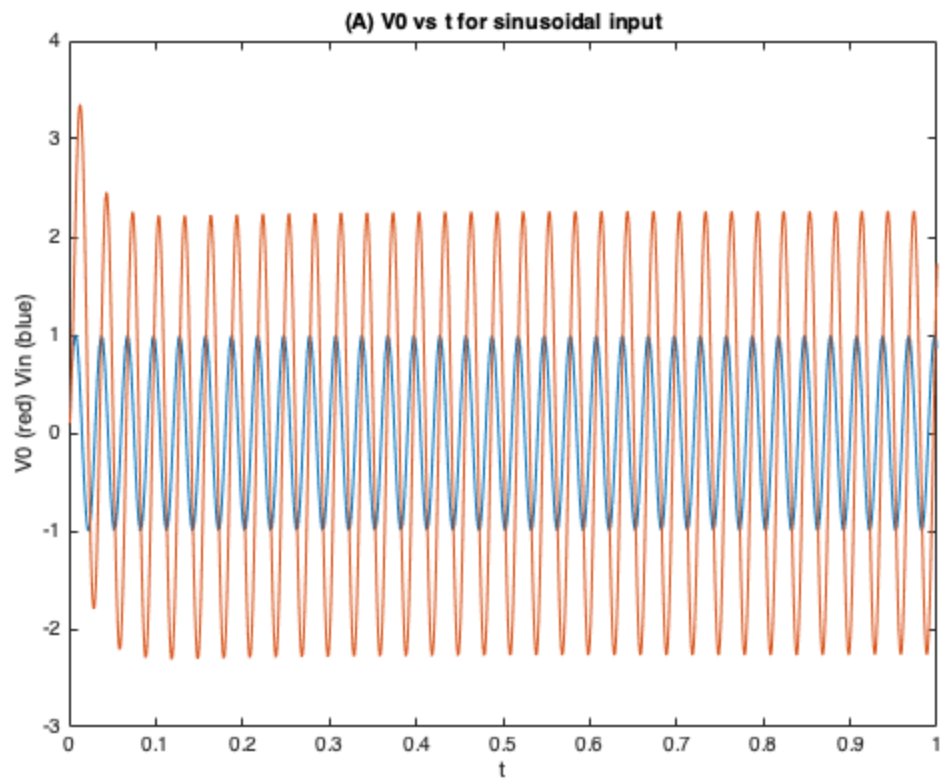


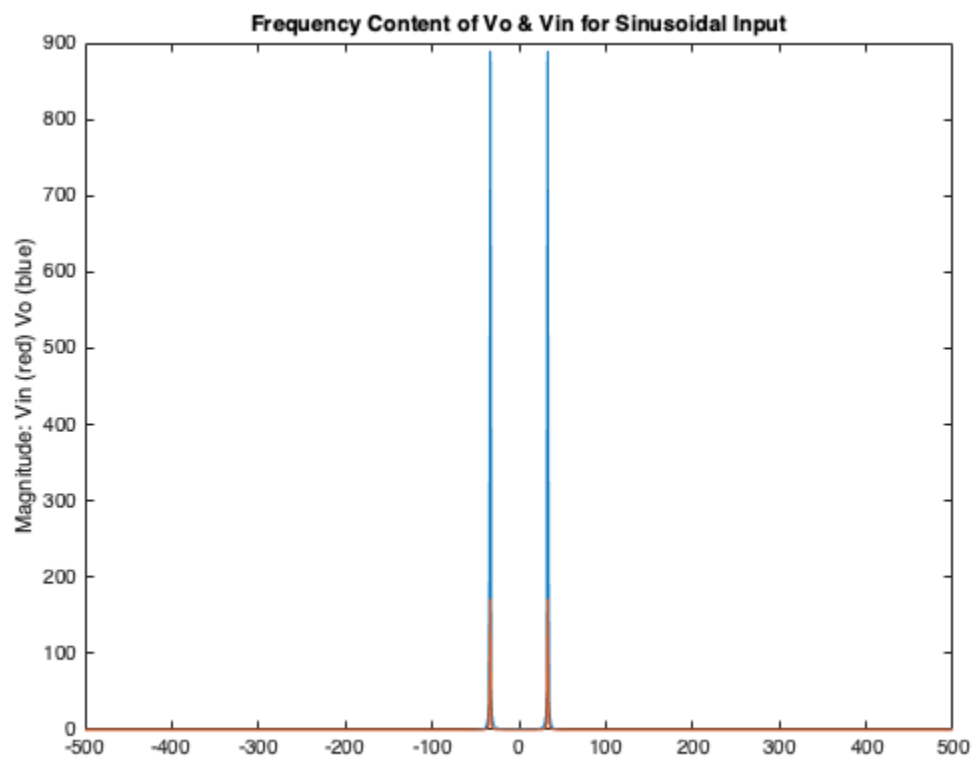
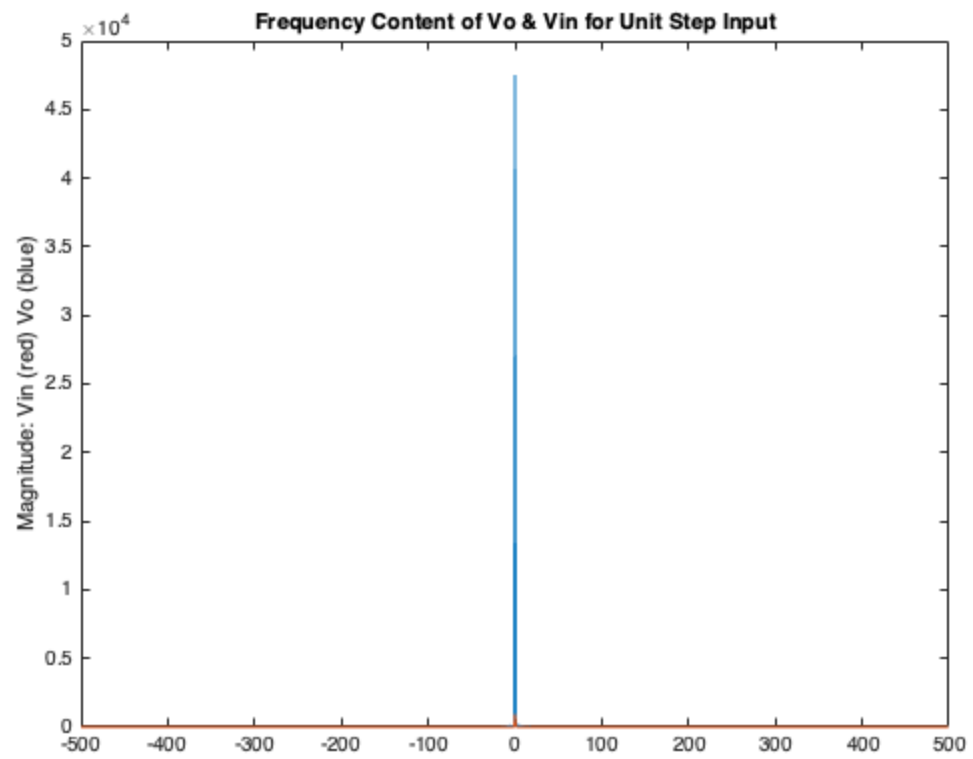


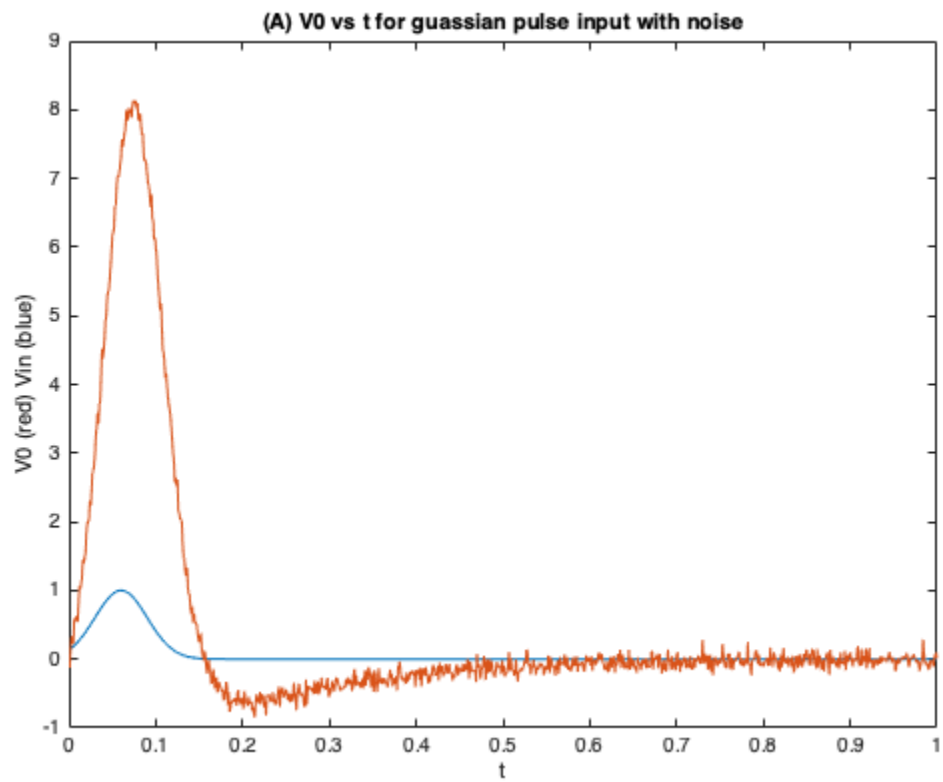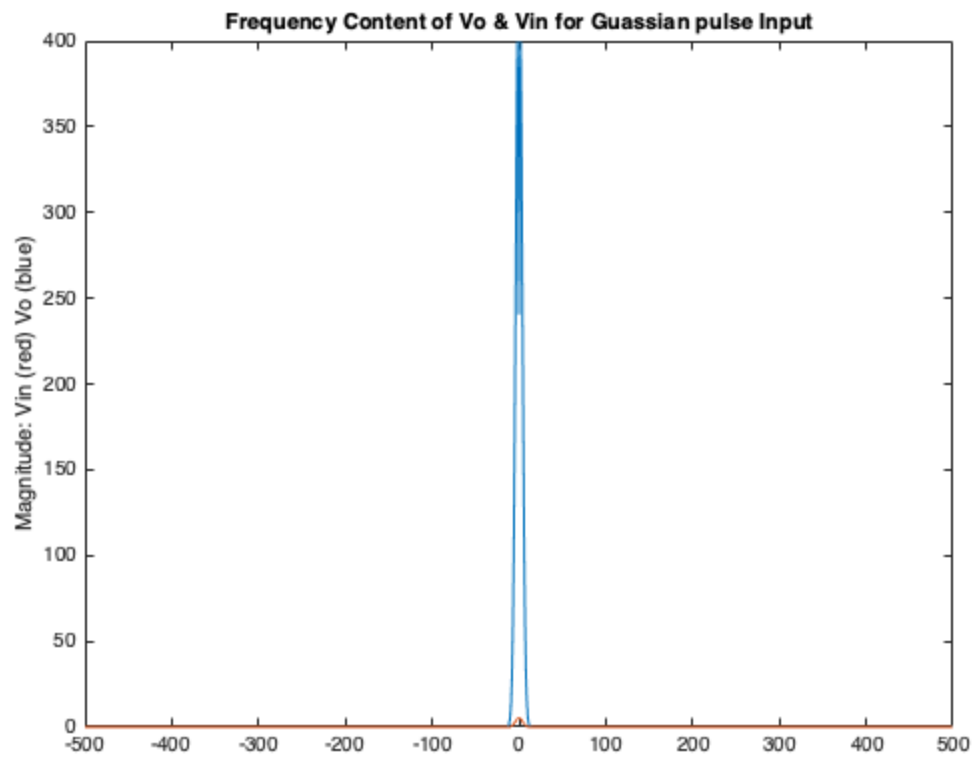


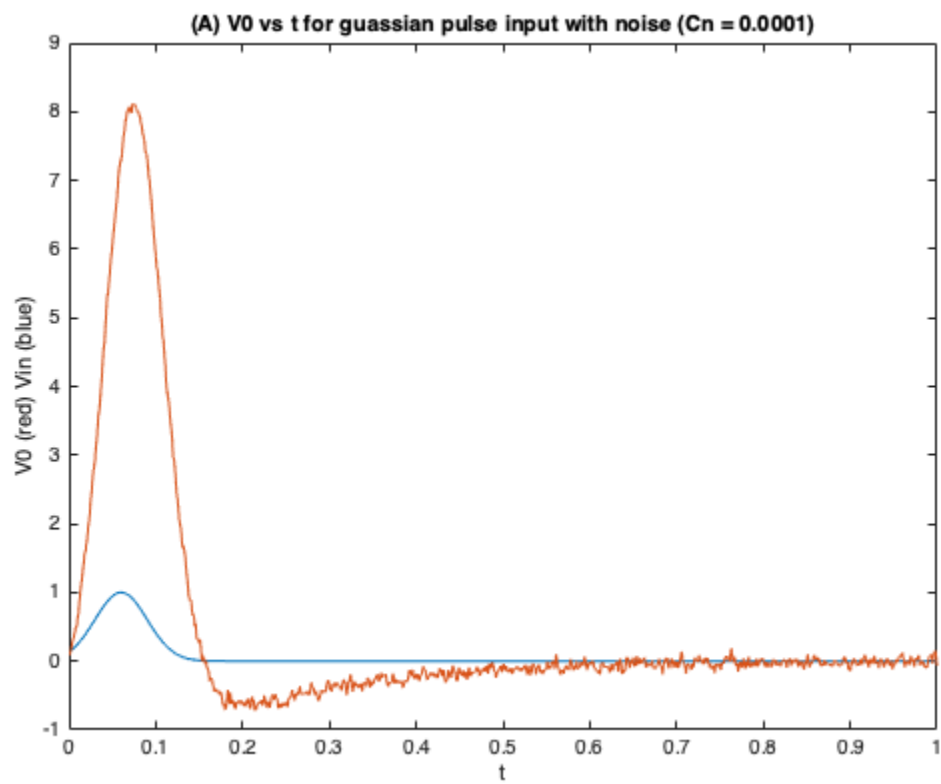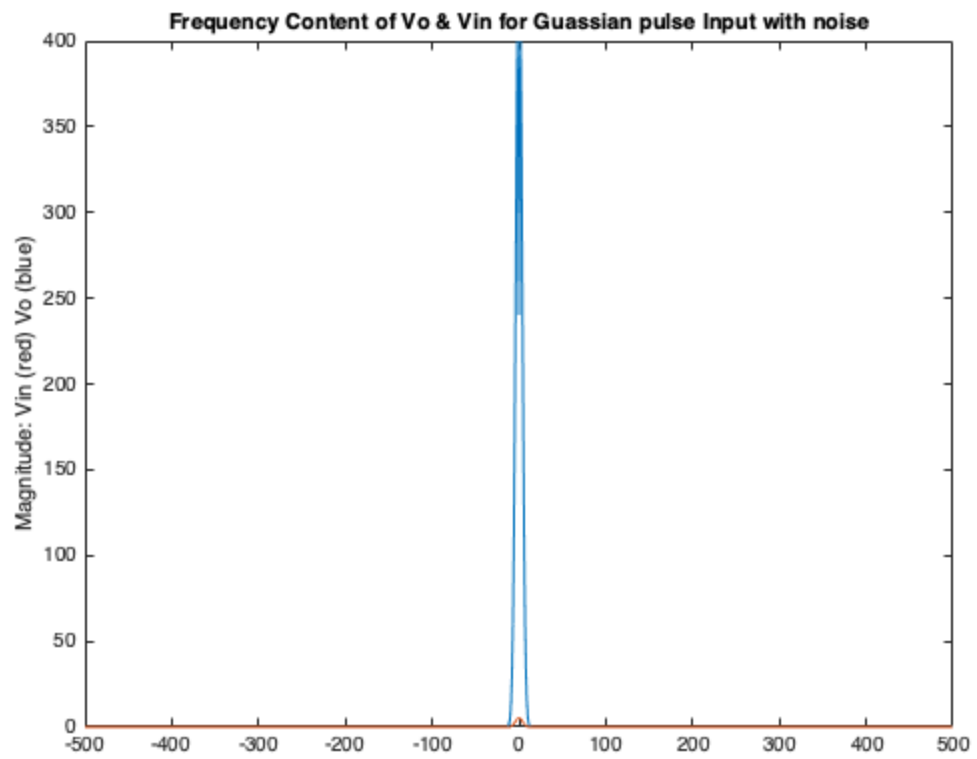

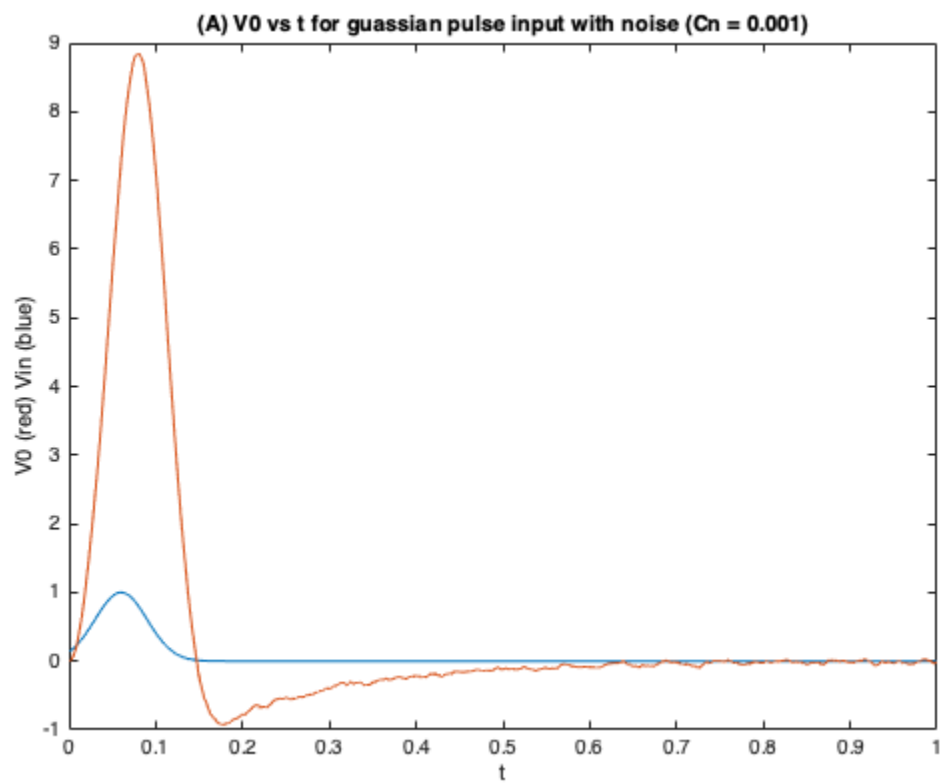

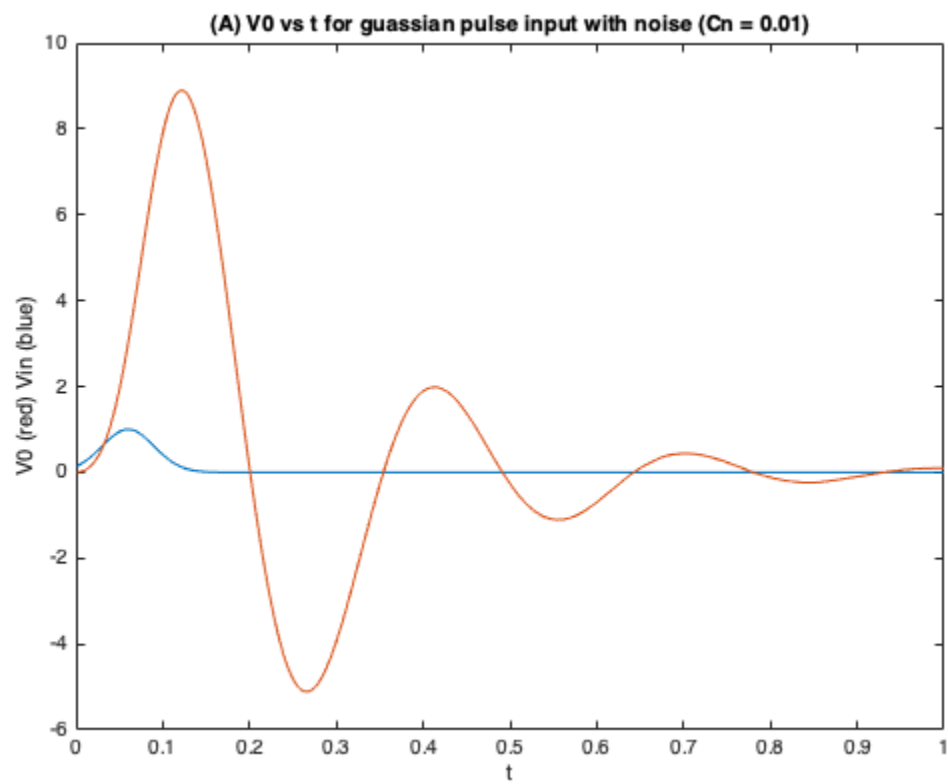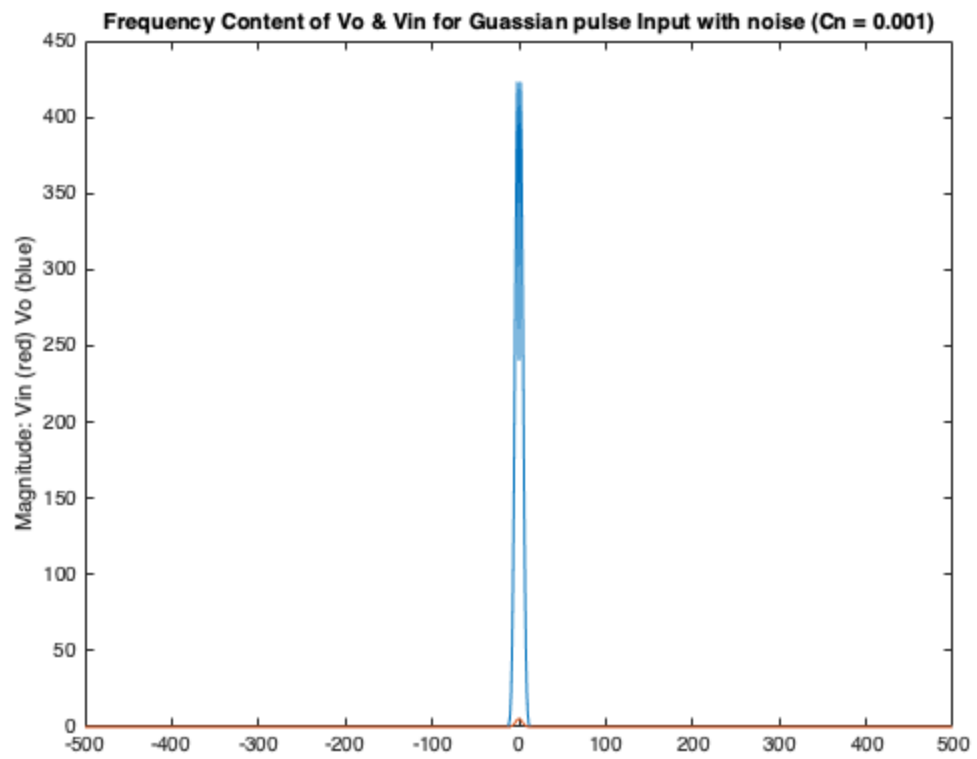

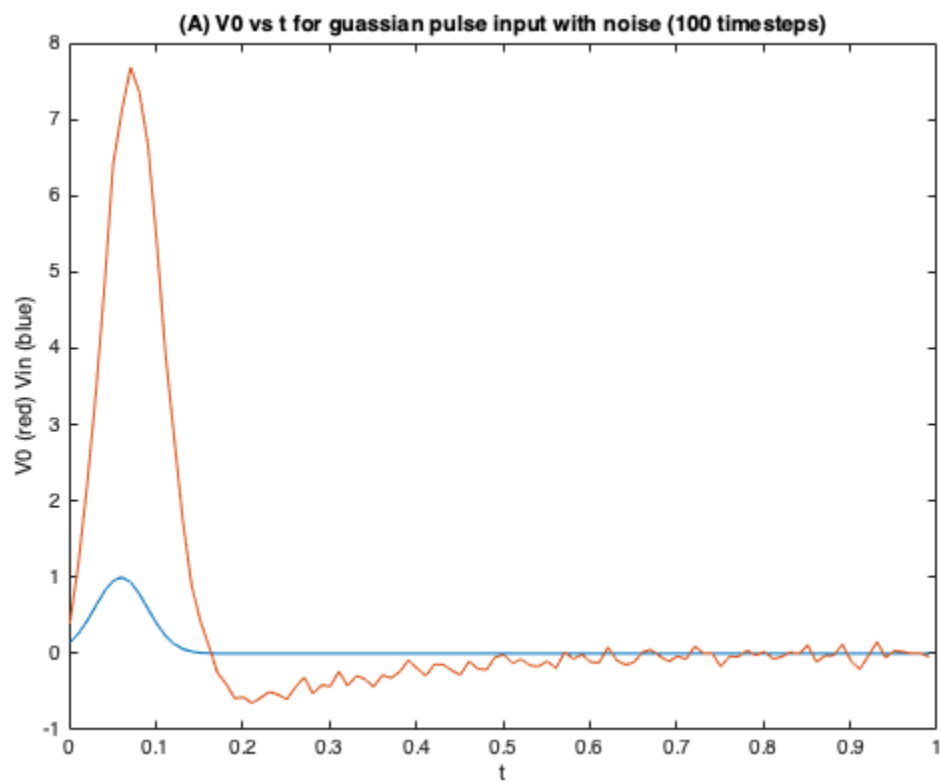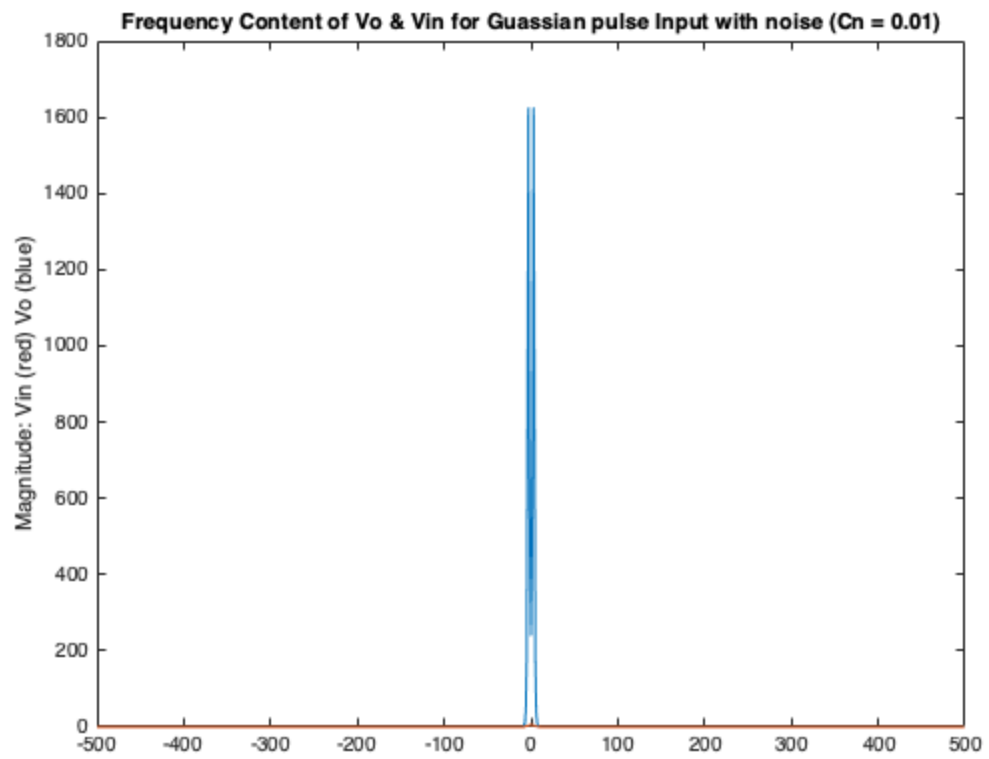

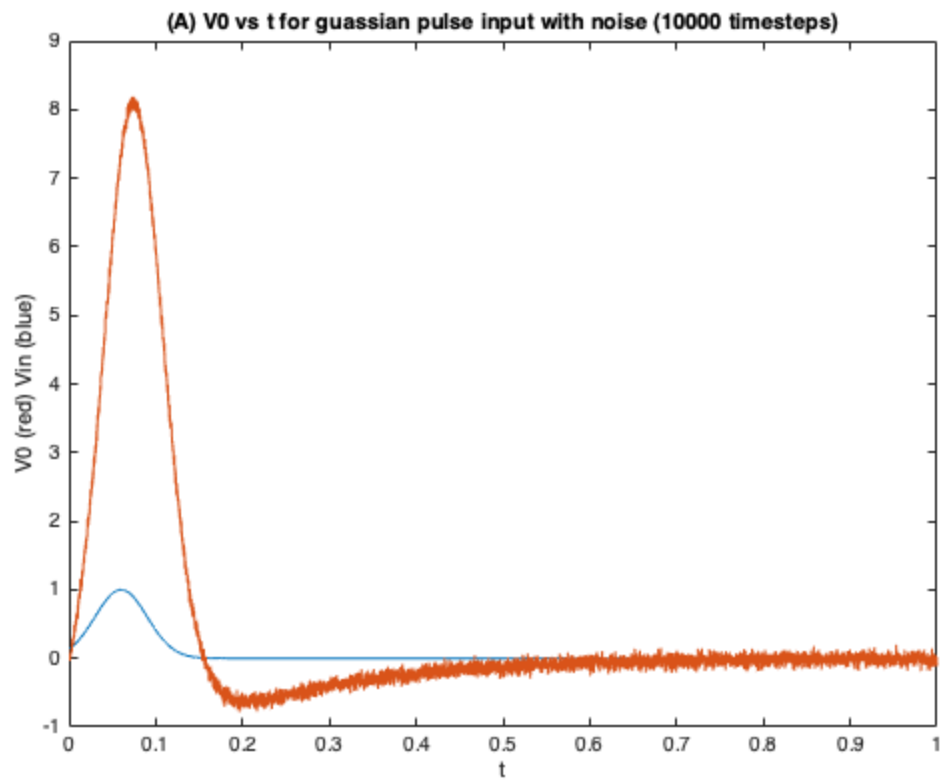

*Published with MATLAB® R2015b*